
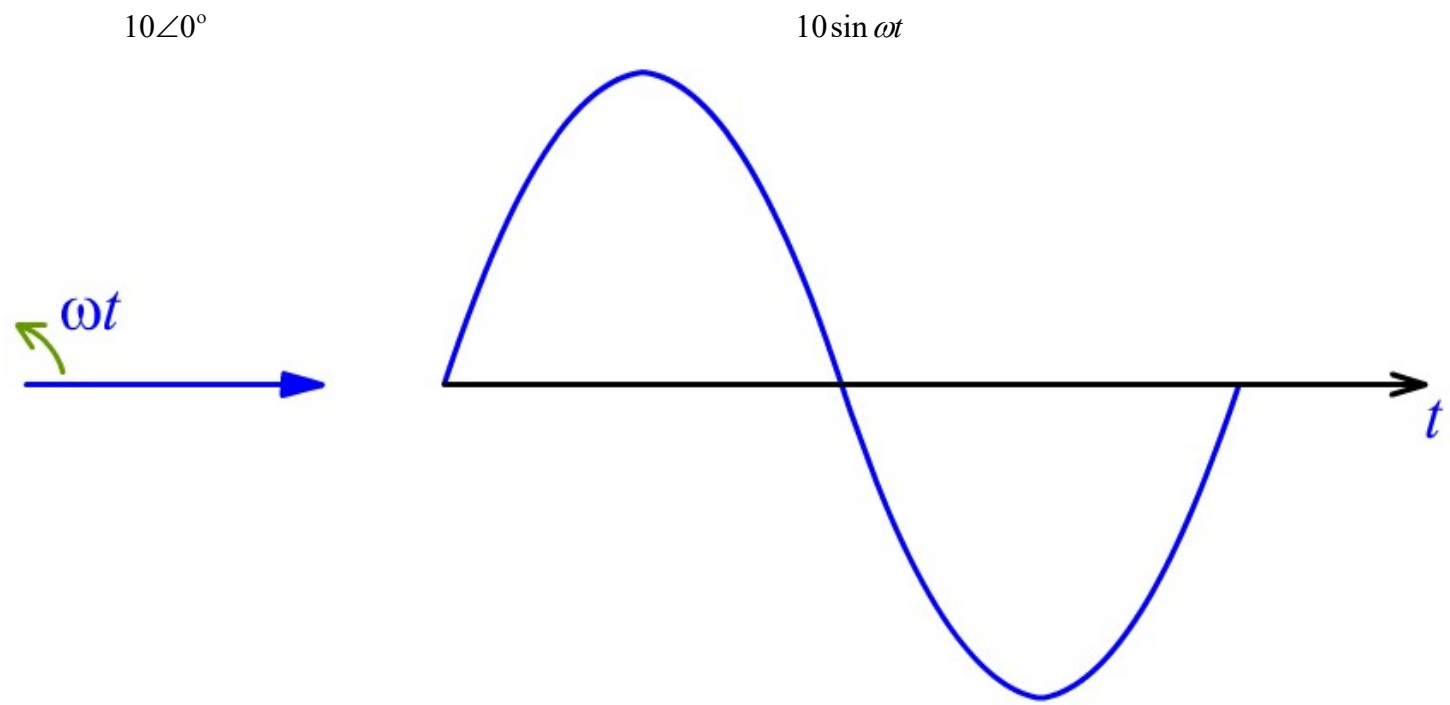


EE2902S



AC Circuits
(Phasor Technique)

Phasor



From t -domain to phasor-domain

- Using Euler's identities,

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$e^{-j\theta} = \cos \theta - j \sin \theta$$

- Assume $\theta = \omega t + \varphi$, we can find the response of a circuit in both cos and sin at the same time.
- Another interesting point is that ωt is always there. We can assume $t = 0$ and solve the problem with φ only. After that just rewrite the solution with $(\omega t + \varphi)$.

From t -domain to phasor-domain

- Using Euler's identities,

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$e^{-j\theta} = \cos \theta - j \sin \theta$$

- For a sine wave, $10\sin(\omega t)$

we can use phasor, $10e^{j0^\circ} = 10\cos 0^\circ + j10\sin 0^\circ$

After solving the problem, write down the answer with either cos or sin.

- Note: polar form expression: $A_1 e^{j\theta} = A_1 \angle \theta$
from polar form to rectangular form:


$$A_1 \angle \theta = A_1 \cos \theta + j A_1 \sin \theta$$

in rad for calculator



Time-domain and phasor technique

Time-domain

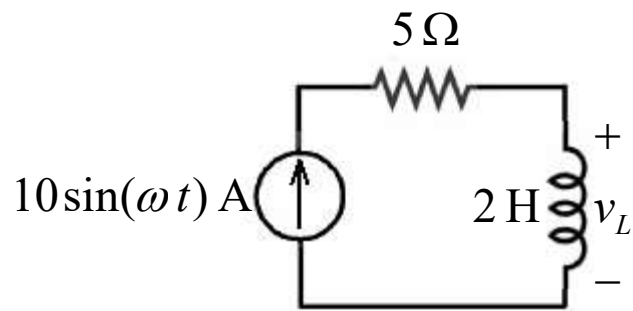


$$\begin{aligned} v_L(t) &= L \frac{di}{dt} \\ &= 2 \frac{d(10\sin(\omega t))}{dt} \\ &= 20\omega \cos(\omega t) \\ &= 20\omega \sin(\omega t + 90^\circ) \end{aligned}$$

Phasor technique

$$I_S = 10\angle 0^\circ \text{ ref : sin}$$

$$Z_L = j\omega L = j2\omega$$

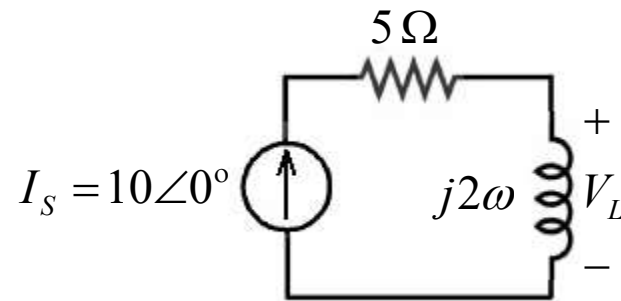


$$V_L = I_S Z_L$$

$$= j20\omega$$

$$v_L(t) = 20\omega \sin(\omega t + 90^\circ)$$

Time-domain and phasor technique

Time-domain

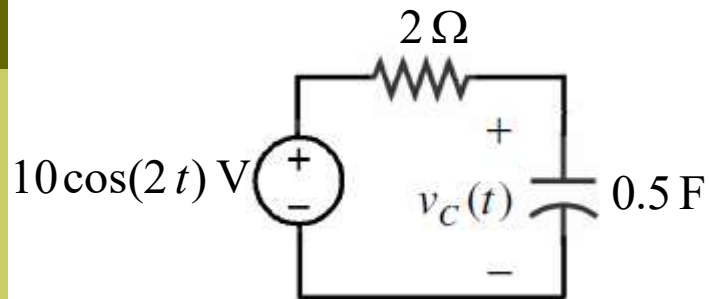

$$i(t) = C \frac{dv_C}{dt}$$

$$\frac{v_s - v_C}{2} = C \frac{dv_C}{dt}$$

$$\frac{10 \cos(2t) - v_C}{2} = 0.5 \frac{dv_C}{dt}$$

$$10 \cos(2t) = \frac{dv_C}{dt} + v_C$$


Solving the differential equation:

$$v_C(t) = 4.472 \cos(2t - 63.43^\circ) \text{ V}$$

Phasor technique

$$V_s = 10 \angle 0^\circ \text{ ref : cos}$$

$$Z_C = \frac{1}{j\omega C} = -1j$$

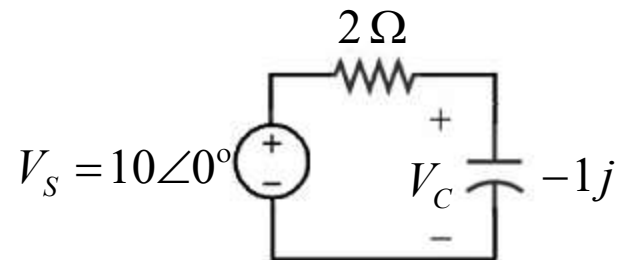

$$V_C = \frac{Z_C}{R + Z_C} V_s$$

$$= \frac{-1j}{2 - 1j} 10 \angle 0^\circ$$

$$= 2 - 4j$$

$$= 4.472 \angle -63.43^\circ$$

$$v_C(t) = 4.472 \cos(2t - 63.43^\circ) \text{ V}$$

CASIO fx-50FH

Before using Complex number calculation, set mode to polar form:

SHIFT **MODE** **►►►** **2** ($r\angle\theta$)

$$V_C = \frac{(-j)}{(2-j)} (10\angle 0^\circ)$$

Press **MODE**.

2

← **COMP** **CMPLX** **BASE** →
1 **2** **3**

(**(-)** **ENG** **(i)** **)** **×** **(** **1** **0** **SHIFT** **(-)** **(∠)** **0** **)** **÷** **(** **2** **-** **ENG** **(i)** **)** **EXE**



4.472135955

SHIFT **EXE** (Re↔Im) **∠** -63.43494882

$$V_C = \underline{\underline{4.472\angle(-63.43^\circ) \text{ V}}}$$

$$v_C(t) = 4.472 \cos(2t - 63.43^\circ) \text{ V}$$

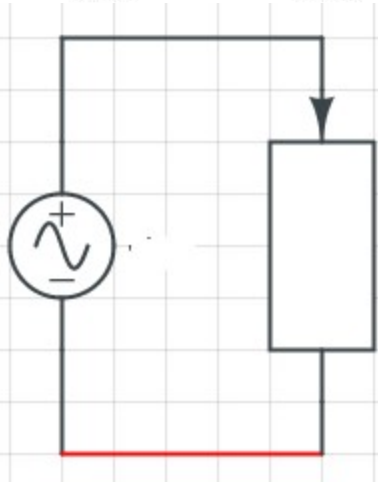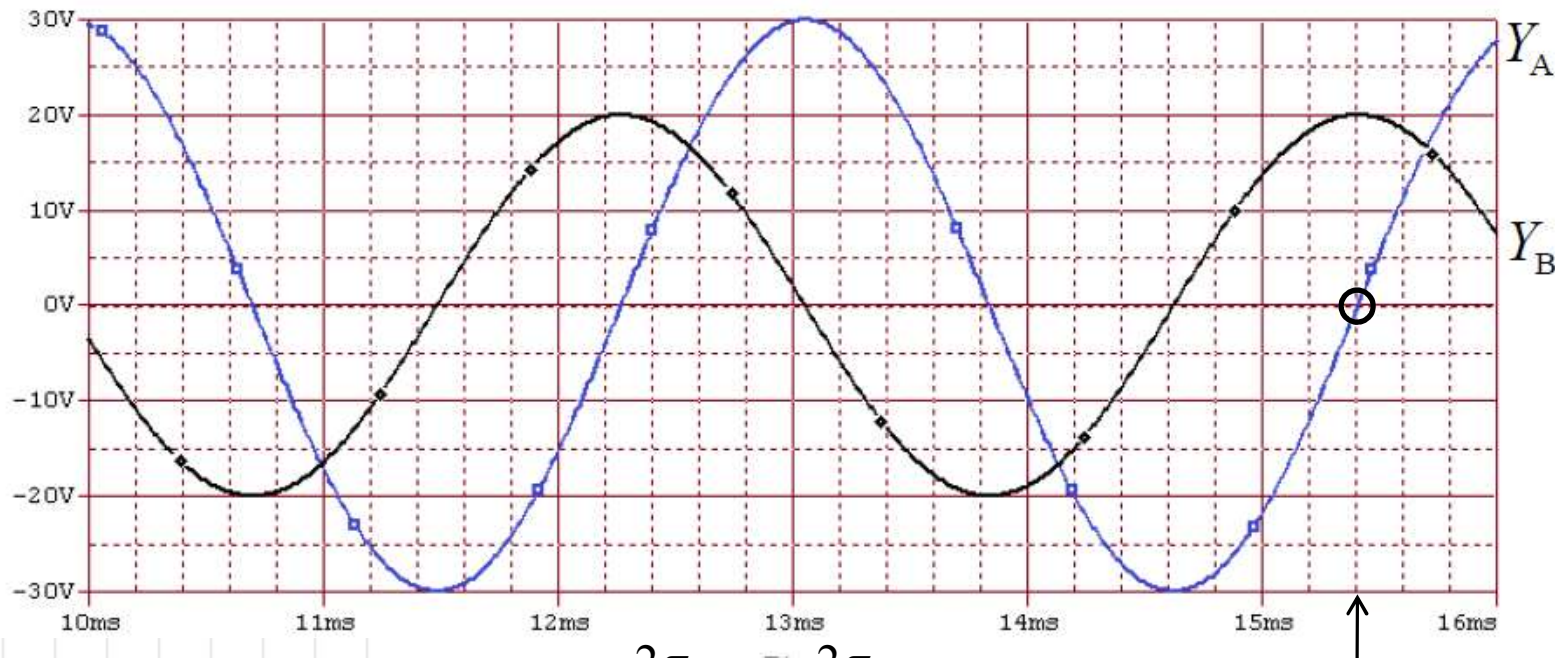If Y_A is voltage and Y_B is current with period $= 3.14 \text{ ms}$, determine the impedance.



$$\omega = 2\pi f = \frac{2\pi}{T} = \frac{2\pi}{3.14 \times 10^{-3}}$$

$$v_s(t) = v_s(t + nT) = v_s(t - nT)$$

$$t = 15.4 \text{ ms} - 4 \times 3.14 \text{ ms} = 2.84 \text{ ms}$$

$$v_s(t) = 30 \sin(\omega t + \theta) \text{ V}$$



$$0 = 30 \sin\left(\left(\frac{2\pi}{3.14 \text{ ms}}\right)(2.84 \text{ ms}) + \theta\right)$$

$$\left(\frac{2\pi}{3.14 \text{ ms}}\right)(2.84 \text{ ms}) + \theta = 0$$

$$\theta = -\frac{2\pi \times 2.84}{3.14} = -325.6^\circ = 34.4^\circ$$

$$\mathbf{V}_s = 30 \angle 34.4^\circ$$

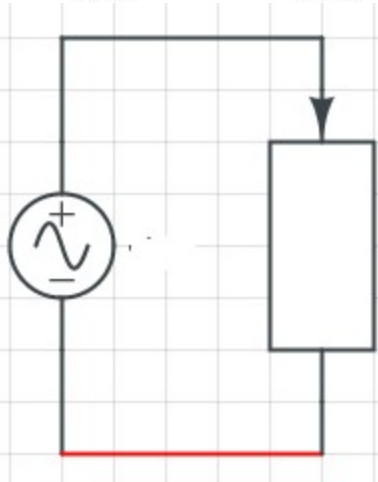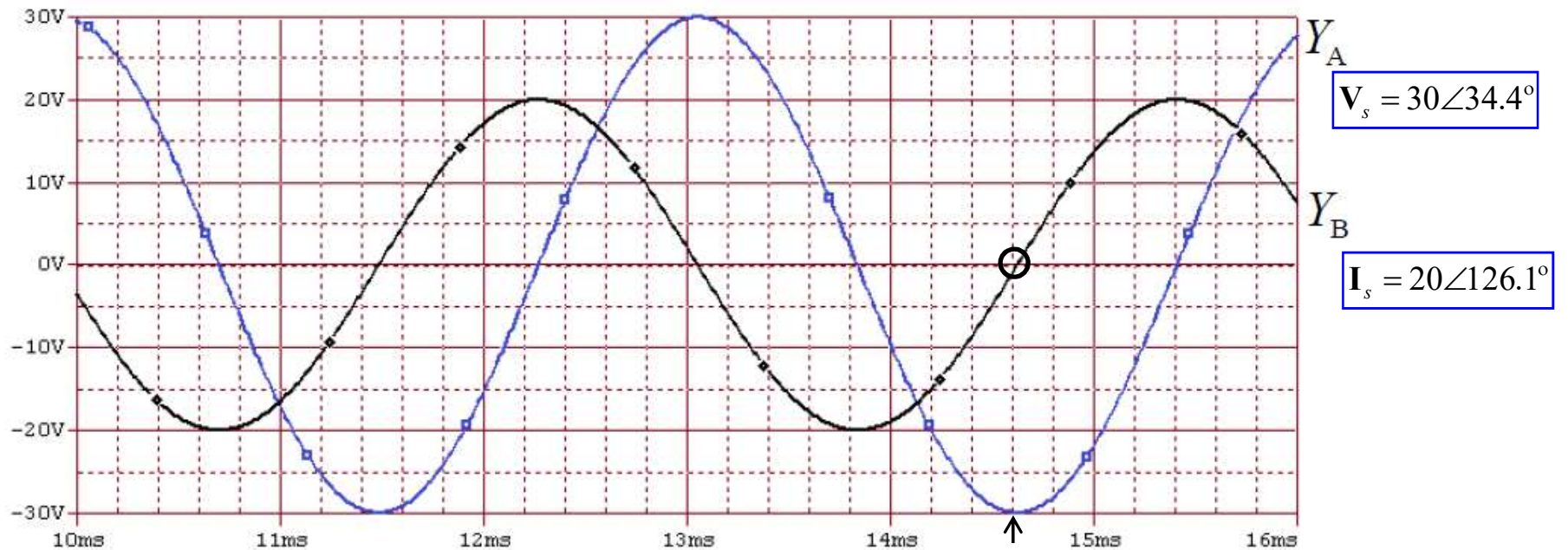If Y_A is voltage and Y_B is current with period $= 3.14 \text{ ms}$, determine the impedance.



$$\omega = 2\pi f = \frac{2\pi}{T} = \frac{2\pi}{3.14 \times 10^{-3}}$$

$$i_s(t) = i_s(t + nT) = i_s(t - nT)$$

$$t = 14.6 \text{ ms} - 4 \times 3.14 \text{ ms} = 2.04 \text{ ms}$$

$$i_s(t) = 20 \sin(\omega t + \phi) \text{ A}$$



$$0 = 20 \sin\left(\left(\frac{2\pi}{3.14 \text{ ms}}\right)(2.04 \text{ ms}) + \phi\right)$$

$$\left(\frac{2\pi}{3.14 \text{ ms}}\right)(2.04 \text{ ms}) + \phi = 0$$

$$\phi = -\frac{2\pi \times 2.04}{3.14} = -233.9^\circ = 126.1^\circ$$

$$I_s = 20 \angle 126.1^\circ$$

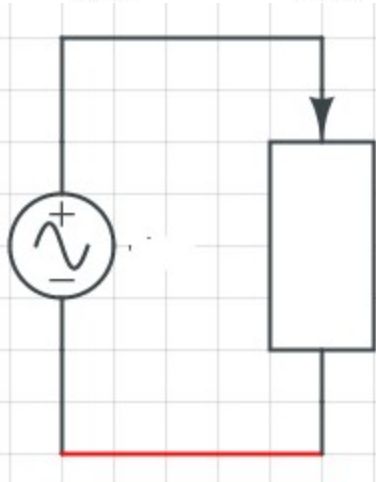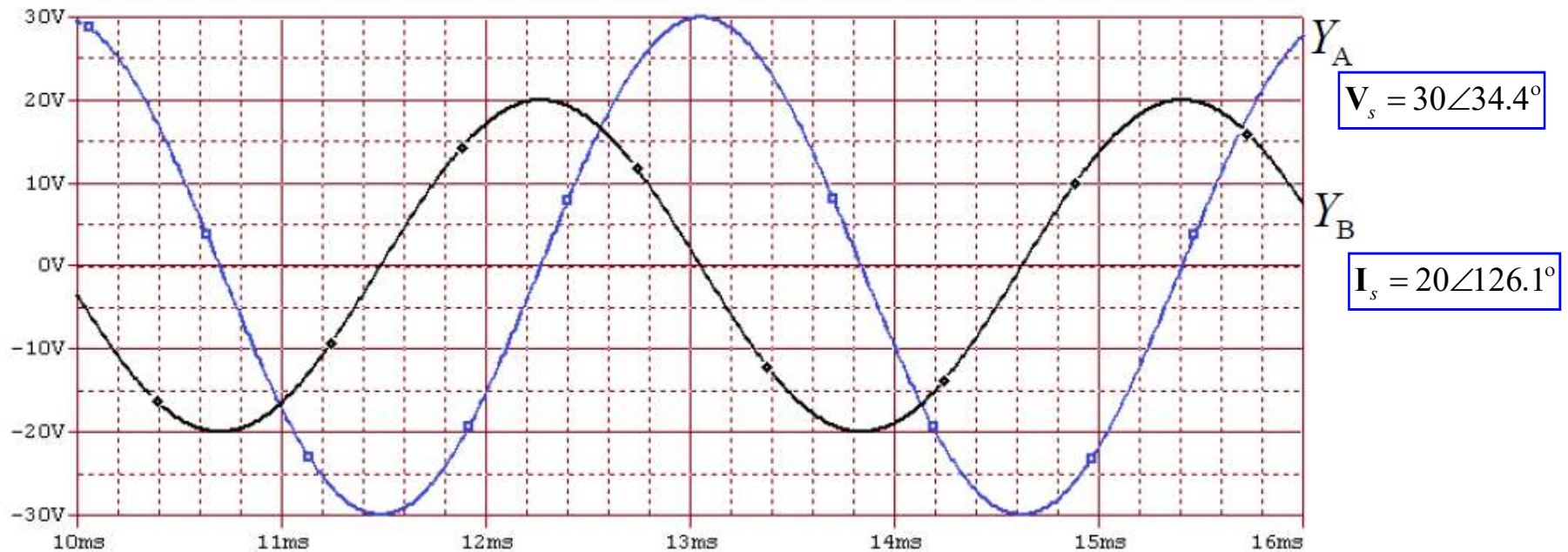If Y_A is voltage and Y_B is current with period $= 3.14 \text{ ms}$, determine the impedance.



$$\omega = 2\pi f = \frac{2\pi}{T} = \frac{2\pi}{3.14 \times 10^{-3}} = 2001.01 \text{ (rad/s)}$$

$$Z = \frac{V_s}{I_s} = \frac{30\angle 34.4^\circ}{20\angle 126.1^\circ} = 1.5\angle -91.7^\circ = -0.044 - j1.499 = R + jX$$

Since $-ve R$ is not possible, this $R = -0.044 \Omega$ should be round off error.

$$-j1.499 = \frac{-j}{\omega C} \Rightarrow C = \frac{1}{1.499\omega} = 0.33 \text{ mF}$$

Q.9 AC Steady State (Phasor)

- ▣ Determine $i_3(t)$ if $i_1(t) = 141.4\cos(377t + 2.356)$ mA
 $i_2(t) = 50\sin(377t - 0.927)$ mA

Using cosine as reference with $\omega = 377$ rad/s


Express $i_1(t)$ and $i_2(t)$ in phasor form,

$$\mathbf{I}_1 = 141.4\angle 2.356 = 141.4\angle 134.99^\circ$$

$$\begin{aligned}\mathbf{I}_2 &= 50\angle (-0.927 - \pi/2) \\ &= 50\angle (-2.4978) \\ &= 50\angle (-143.11^\circ)\end{aligned}$$

$$\begin{aligned}\mathbf{I}_3 &= \mathbf{I}_1 - \mathbf{I}_2 \\ &= 141.4\angle 134.99^\circ - 50\angle (-143.11^\circ) \\ &= 143.1839\angle 114.76^\circ\end{aligned}$$

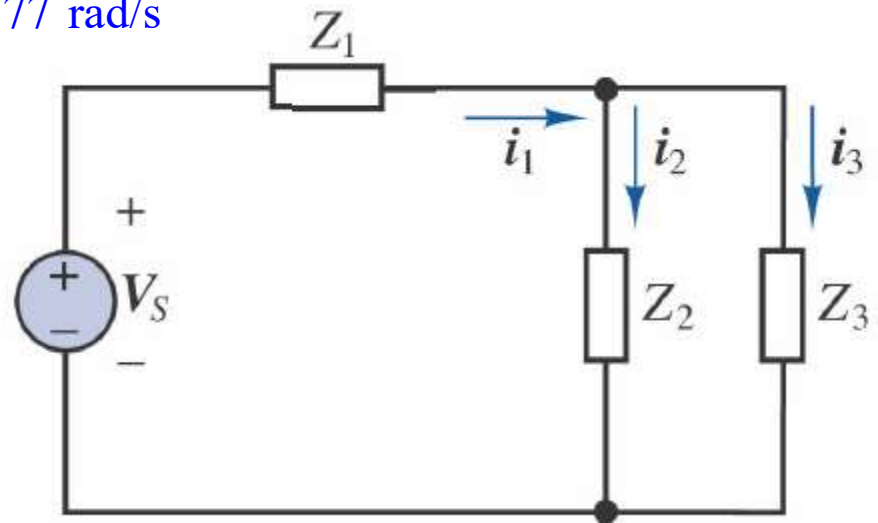Convert to time domain, $i_3(t) = 143.1839\cos(377t + 114.76^\circ)$ mA



Q.10 AC Steady State

$$\frac{A\angle\theta}{B\angle\phi} = (A/B) \angle (\theta - \phi)$$


- Determine the frequency so that the current \mathbf{I}_i and the voltage \mathbf{V}_o are in phase.

Only pure resistance with current and voltage in phase,

$$\begin{aligned}
 Z_{eq} &= \frac{1}{j\omega C} \parallel (R + j\omega L) = \frac{\left(\frac{1}{j\omega C}\right)(R + j\omega L)}{\frac{1}{j\omega C} + R + j\omega L} \\
 &= \frac{R + j\omega L}{1 + j\omega CR - \omega^2 CL} = \frac{R + j\omega L}{(1 - \omega^2 CL) + j\omega CR}
 \end{aligned}$$

The phase angle of $Z_{eq} = 0$

$$\begin{aligned}
 \frac{\omega L}{R} = \frac{\omega CR}{1 - \omega^2 CL} \quad & \left| \quad \omega = \sqrt{\frac{1}{CL} - \frac{R^2}{L^2}} \right. \\
 1 - \omega^2 CL = \frac{CR^2}{L} \quad & \left| \quad = \sqrt{\frac{1}{(220 \times 10^{-12})(0.019)} - \frac{120^2}{0.019^2}} = \underline{\underline{489.075 \text{ (krad/s)}}}
 \end{aligned}$$

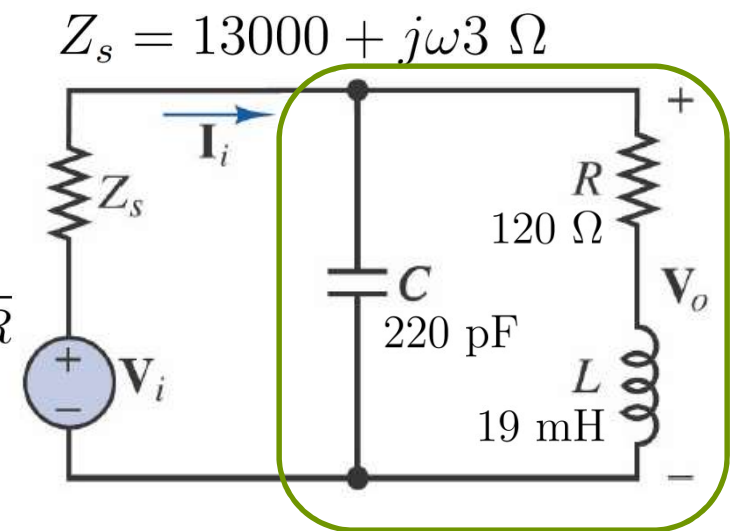

Make this part becomes pure resistance.

Q.13 AC Steady State

- Solve for $v_2(t)$ and show the answer in time domain.

Given that $v_s(t) = 25\sin(2t)$ V


From the given voltage source, use $\sin(\omega t)$ as reference

In phasor domain, $\mathbf{V}_s = 25\angle 0^\circ$ $\omega = 2$ rad/s

Apply voltage divider equation,

$$\begin{aligned}\mathbf{V}_2 &= \frac{6}{12 + j\omega 6 + 6} \times \mathbf{V}_s \\ &= \left(\frac{6}{18 + j12} \right) (25\angle 0^\circ) \\ &= 6.9337\angle (-33.69^\circ)\end{aligned}$$

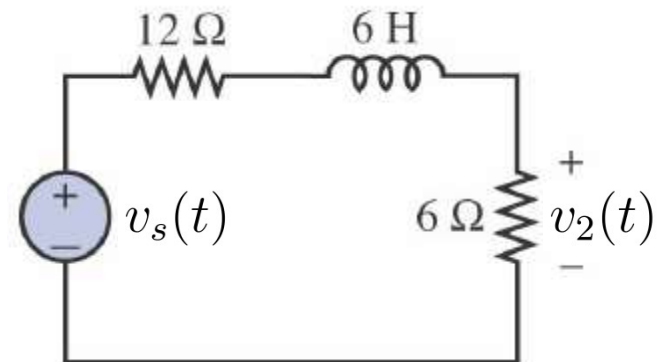Convert to time domain, $v_2(t) = \underline{\underline{6.9337\sin(2t - 33.69^\circ) \text{ (V)}}}$



CASIO fx-50FH

Before using Complex number calculation set mode to polar form:

SHIFT **MODE** **▶** **▶** **▶** **2** ($r\angle\theta$)

$$V_2 = \left(\frac{6}{18 + j12} \right) (25\angle 0)$$

Press **MODE**.

2

← **COMP** **CMPLX** **BASE** →
1 **2** **3**

6 **X** **(** **2** **5** **SHIFT** **(-)** **(∠)** **0** **)** **÷** **(** **1** **8** **+** **1** **2** **ENG** **(i)** **)** **EXE**


6.933752453

SHIFT **EXE** (Re↔Im) **∠** -33.69006753

$$V_2 = \underline{\underline{6.9337\angle(-33.69^\circ) \text{ V}}}$$

AC Steady State

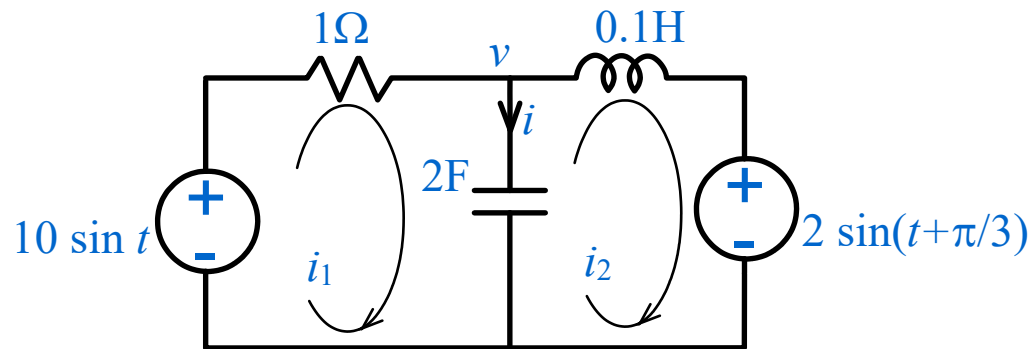- Use the mesh-current method to solve the circuit. Convert all voltages and currents to the form $X \sin(t + \phi)$. You need only find the steady-state solutions.



AC Steady State (Phasor)

Apply KVL for loop i_1 ,

$$-10\angle 0^\circ + 1 \times \mathbf{I}_1 + \frac{-j}{2}(\mathbf{I}_1 - \mathbf{I}_2) = 0$$

$$(1 - j0.5)\mathbf{I}_1 + j0.5\mathbf{I}_2 = 10$$

Apply KVL for loop i_2 ,

$$2\angle 60^\circ + \frac{-j}{2}(\mathbf{I}_2 - \mathbf{I}_1) + j0.1 \times \mathbf{I}_2 = 0$$

$$-j0.5\mathbf{I}_1 + j0.4\mathbf{I}_2 = 1 + j1.732051$$


$$\Delta = \begin{vmatrix} 1 - j0.5 & j0.5 \\ -j0.5 & j0.4 \end{vmatrix} = (1 - j0.5) \times j0.4 + j0.5 \times j0.5$$

$$= -0.05 + j0.4$$

$$\Delta_1 = \begin{vmatrix} 10 & j0.5 \\ 1 + j1.732051 & j0.4 \end{vmatrix} = 10 \times j0.4 - (1 + j1.732051) \times j0.5$$

$$= 0.8660255 + j3.5$$

consider $\sin \omega t$ as reference

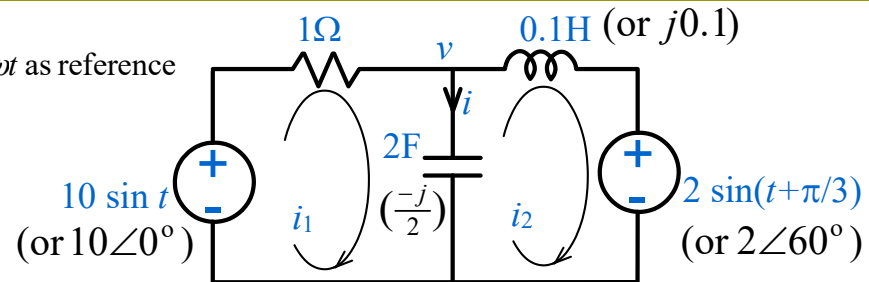

$$\begin{cases} (1 - j0.5)\mathbf{I}_1 + j0.5\mathbf{I}_2 + (0)\mathbf{I}_3 = 10 \\ -j0.5\mathbf{I}_1 + j0.4\mathbf{I}_2 + (0)\mathbf{I}_3 = 1 + j1.732051 \\ \mathbf{I}_3 = 1 \end{cases}$$

Using *fx-50FH* calculator enter the following:

Press Prog1 and then press:

1-0.5 i EXE 0.5 i EXE 0 EXE 10 EXE

-0.5 i EXE 0.4 i EXE 0 EXE 1 + 1.732051 i EXE

0 EXE 0 EXE 1 EXE 1 EXE (*disp I₁*) EXE (*disp I₂*) EXE (*disp 1*).

RCL A (*disp I₁*) SHIFT r∠θ EXE (*disp I₁* in polar form).

RCL B (*disp I₂*) SHIFT r∠θ EXE (*disp I₂* in polar form).

$$\mathbf{I}_1 = \frac{\Delta_1}{\Delta} = \frac{0.8660255 + j3.5}{-0.05 + j0.4} = 8.944271 \angle (-21.0229^\circ)$$

Convert to time-domain notation,

$$i_1(t) = 8.944271 \sin(t - 21.0229^\circ) \text{ A}$$


Q.4 AC Steady State (Phasor)

$$\Delta = \begin{vmatrix} 1-j0.5 & j0.5 \\ -j0.5 & j0.4 \end{vmatrix} = -0.05 + j0.4$$

$$\begin{aligned} \Delta_2 &= \begin{vmatrix} 1-j0.5 & 10 \\ -j0.5 & 1+j1.732051 \end{vmatrix} \\ &= (1-j0.5) \times (1+j1.732051) + (j0.5) \times 10 \\ &= 1.866026 + j6.232051 \end{aligned}$$

$$\begin{aligned} \mathbf{I}_2 &= \frac{\Delta_2}{\Delta} = \frac{1.866026 + j6.232051}{-0.05 + j0.4} \\ &= 16.137961 \angle (-23.794^\circ) \end{aligned}$$
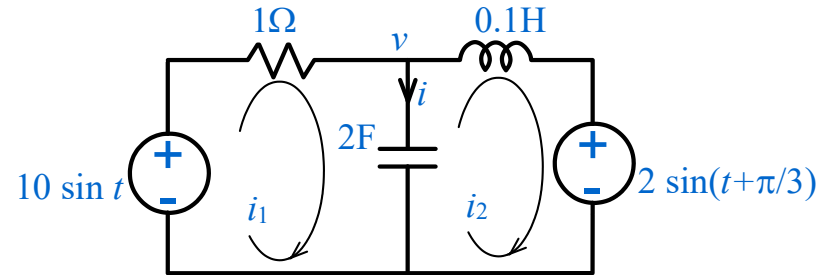
$$i_2(t) = 16.137961 \sin(t - 23.794^\circ) \text{ A}$$



$$\mathbf{I} = (\mathbf{I}_1 - \mathbf{I}_2)$$

$$= 8.944271 \angle -21.0229^\circ - 16.137961 \angle -23.794^\circ$$

$$= 7.217114 \angle 152.771^\circ$$

$$i(t) = 7.217114 \sin(t + 152.771^\circ) \text{ A}$$





$$\mathbf{V} = (\mathbf{I}) \left(\frac{-j}{2} \right)$$

$$= (7.217114 \angle 152.771^\circ) \times (0.5 \angle -90^\circ)$$


$$= 3.608557 \angle 62.771^\circ$$

$$v(t) = 3.608557 \sin(t + 62.771^\circ) \text{ V}$$

root-mean-square value

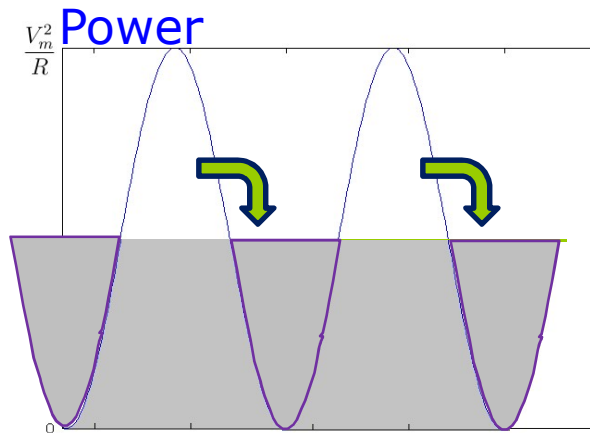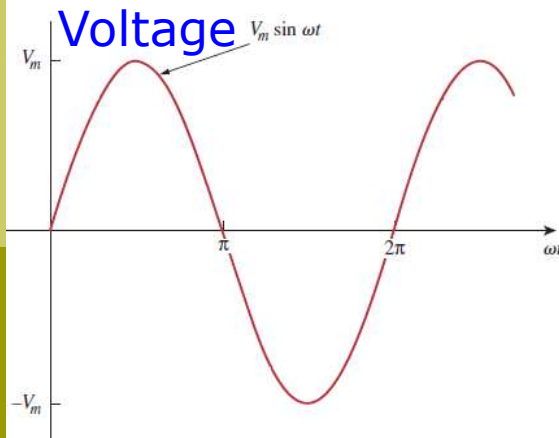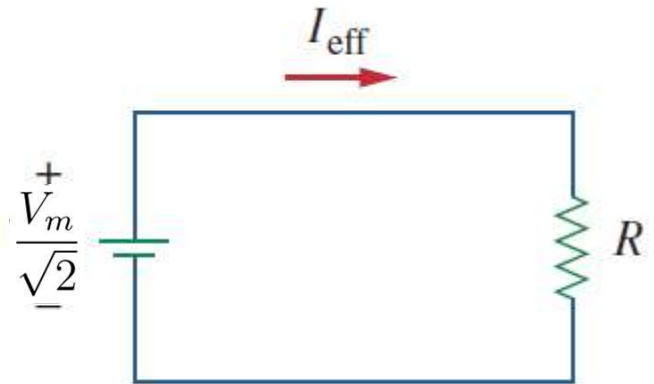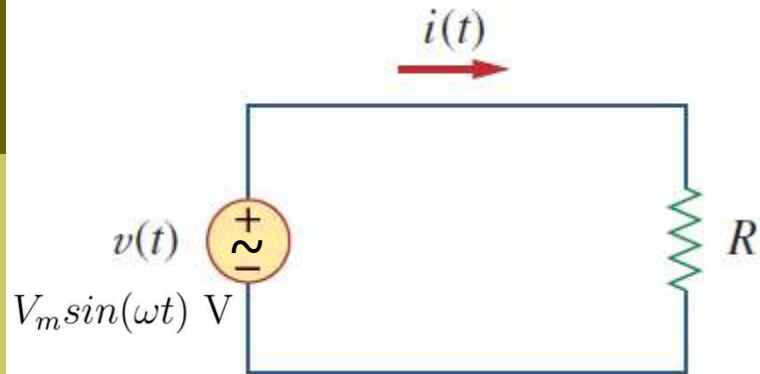
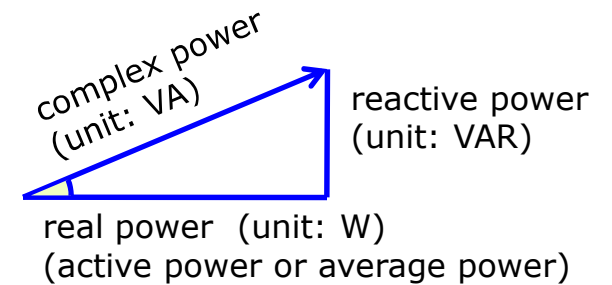
$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T (V_m \sin(\omega t))^2 dt} = \frac{V_m}{\sqrt{2}}$$



$$\text{At time } t, \text{ power} = \frac{v(t)^2}{R} = \frac{V_m^2 \sin^2(\omega t)}{R}$$

$$\text{Average power} = \frac{V_m^2}{2R} = \frac{(V_m/\sqrt{2})^2}{R}$$

$$\mathbf{S} = P + jQ$$

$$|\mathbf{S}| = \text{apparent power (unit: VA)}$$

$$\cos \theta = \text{power factor}$$

SHIFT MODE ►►► 2 ($r\angle\theta$)

Press MODE 2

AC Power #1


(1 0 0 SHIFT (→) (∠) 2 5) SHIFT = (► $a+bi$) EXE
SHIFT EXE (Re↔Im)

- The current flowing in an impedance, Z_L , is $10 \sin(\omega t - 10^\circ)$ A, and the voltage across it is $20 \sin(\omega t + 15^\circ)$ V. Calculate the complex power, real power, and reactive power in the impedance. What is the power factor of Z_L ? Find Z_L .

Given $i = 10 \sin(\omega t - 10^\circ)$ A

$v = 20 \sin(\omega t + 15^\circ)$ V

Sketch the phasors: I lags V by 25°

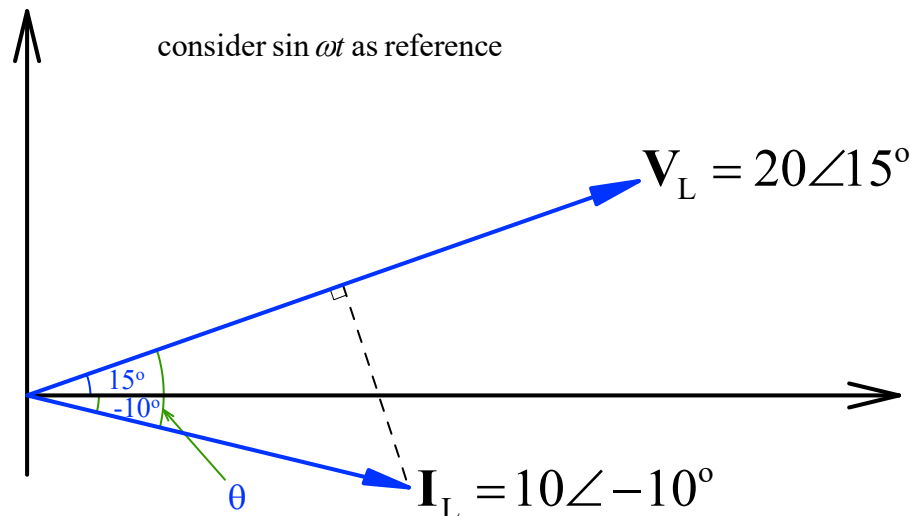

Complex power

$$\begin{aligned} S_L &= \tilde{V}_L \tilde{I}_L^* \\ &= \left(\frac{20\angle 15^\circ}{\sqrt{2}} \right) \times \left(\frac{10\angle 10^\circ}{\sqrt{2}} \right) \\ &= 100\angle 25^\circ \text{ VA} \\ &= 90.63 + j42.26 \text{ VA} \end{aligned}$$

Real power (or average power)

$$P = \text{Re}\{S\} = 90.63 \text{ W}$$

Reactive power

$$Q = \text{Im}\{S\} = 42.26 \text{ VAR}$$



Power factor of Z_L

$$= \cos(25^\circ) = 0.9063 \text{ (lagging)}$$

AC Power #1




To find Z_L , I lags $V \Rightarrow$ inductive load.
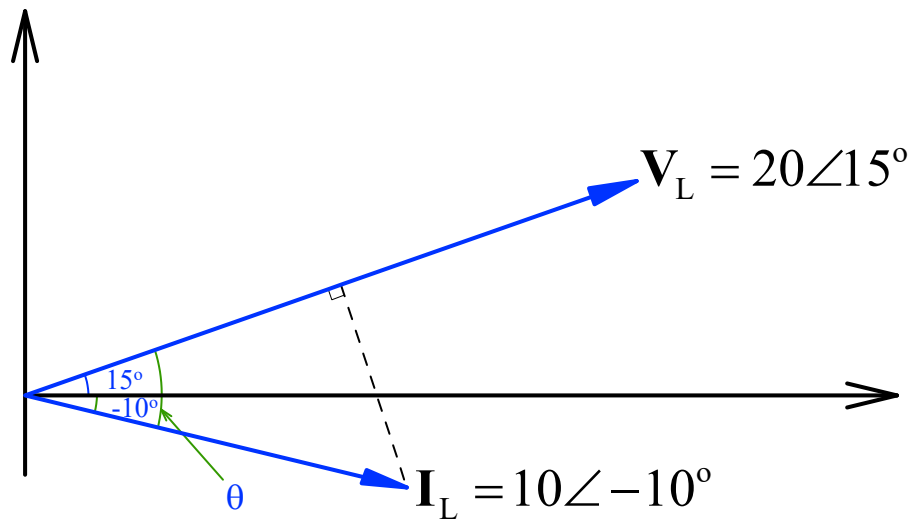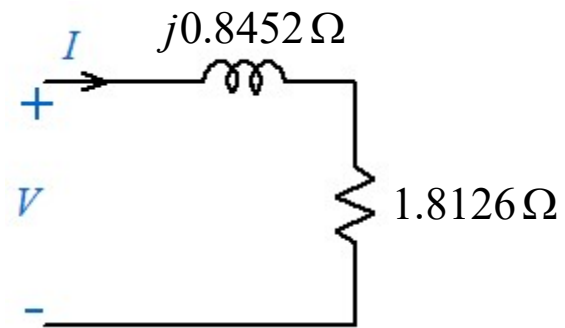
$$\begin{aligned} Z_L &= \frac{\mathbf{V}_L}{\mathbf{I}_L} \\ &= \frac{20\angle 15^\circ}{10\angle -10^\circ} \\ &= 1.8126 + j0.8452 \, \Omega \end{aligned}$$



AC Power #2

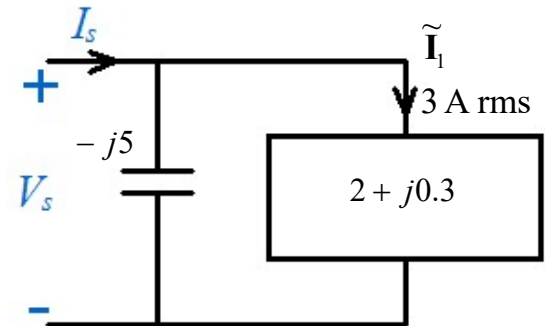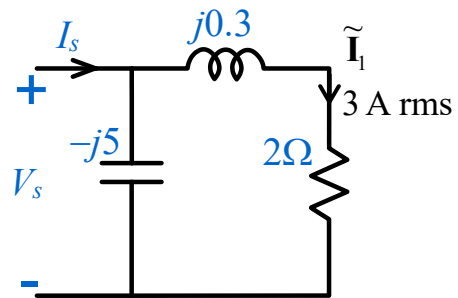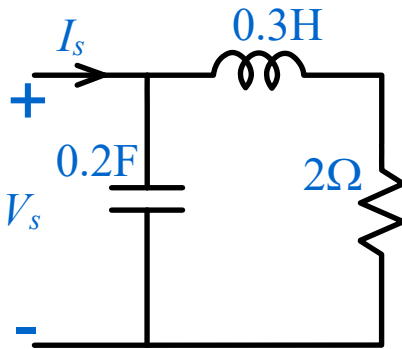
- The current through the resistor is 3 A rms. What are the input current and voltage, assume the driving angular frequency is 1 rad/s? Calculate the input active, reactive, and apparent powers, and hence the input power factor.



AC Power #2

Apply current divider equation,
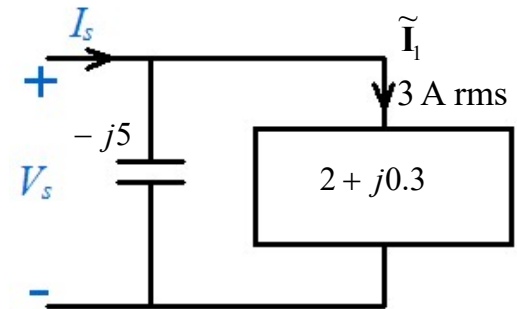
$$\begin{aligned} 3 &= \left(\frac{-j5}{-j5 + 2 + j0.3} \right) (\tilde{\mathbf{I}}_s) \\ &= \left(\frac{-j5}{2 - j4.7} \right) (\tilde{\mathbf{I}}_s) \\ \tilde{\mathbf{I}}_s &= \frac{3(2 - j4.7)}{-j5} \\ &= \frac{6 - j14.1}{-j5} \\ &= \frac{15.3235 \angle -66.95^\circ}{5 \angle -90^\circ} \\ &= 3.0647 \angle 23.05^\circ \end{aligned}$$



By Ohm's law,

$$\begin{aligned} \tilde{\mathbf{V}}_s &= (\tilde{\mathbf{I}}_1)(2 + j0.3) \\ &= 3(2 + j0.3) \\ &= 6 + j0.9 \\ &= 6.0671 \angle 8.53^\circ \end{aligned}$$

Complex power

$$\begin{aligned} \mathbf{S} &= \tilde{\mathbf{V}}_s \tilde{\mathbf{I}}_s^* \\ &= (6.0671 \angle 8.53^\circ)(3.0647 \angle (-23.05^\circ)) \\ &= (6.0671 \times 3.0647) \angle (8.53^\circ - 23.05^\circ) \\ &= 18.5939 \angle (-14.52^\circ) \text{ VA} \end{aligned}$$

AC Power #2

Complex power,

$$\begin{aligned} \mathbf{S} &= 18.5939 \angle (-14.52^\circ) \\ &= 18.5939 \cos(-14.52^\circ) + j18.5939 \sin(-14.52^\circ) \\ &= 18 - j4.662 \end{aligned}$$

Real power,


$$P = 18 \text{ W}$$

Reactive power,

$$Q = -4.662 \text{ VAR}$$

Apparent power,

$$|\mathbf{S}| = 18.5939 \text{ (VA)}$$

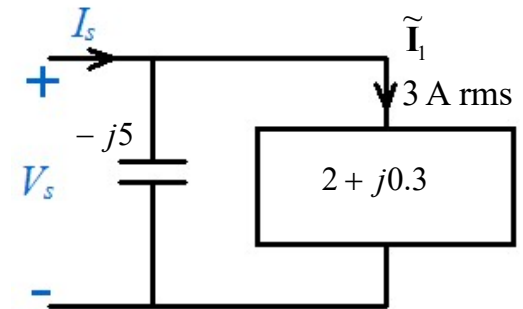


The power factor is

$$\begin{aligned} \text{p.f.} &= \cos(-14.52^\circ) \\ &= 0.9681 \text{ (leading)} \end{aligned}$$


Leading means "I leads V."

Phase and Line Voltages

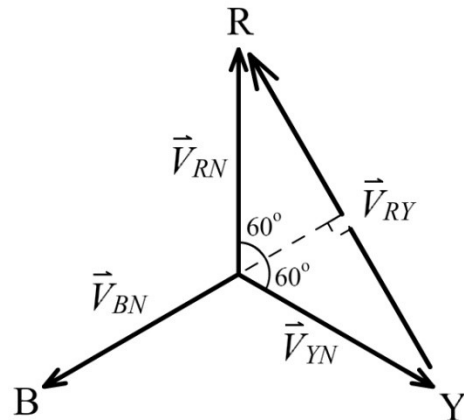- Find the phase voltage V_P in terms of line voltage V_L . $\vec{V}_{RN} = V_P \angle 0^\circ$, $\vec{V}_{BN} = V_P \angle 120^\circ$, and $\vec{V}_{YN} = V_P \angle -120^\circ$
- If $V_L = 380$ V, what is V_P ?
Draw the voltage diagram as follows:



$$\begin{aligned}
 V_L &= |\vec{V}_{RY}| = |\vec{V}_{RN}| \sin 60^\circ + |\vec{V}_{YN}| \sin 60^\circ \\
 &= V_P \sin 60^\circ + V_P \sin 60^\circ \\
 &= 2V_P \sin 60^\circ = 2V_P \left(\frac{\sqrt{3}}{2} \right) = \sqrt{3}V_P
 \end{aligned}$$

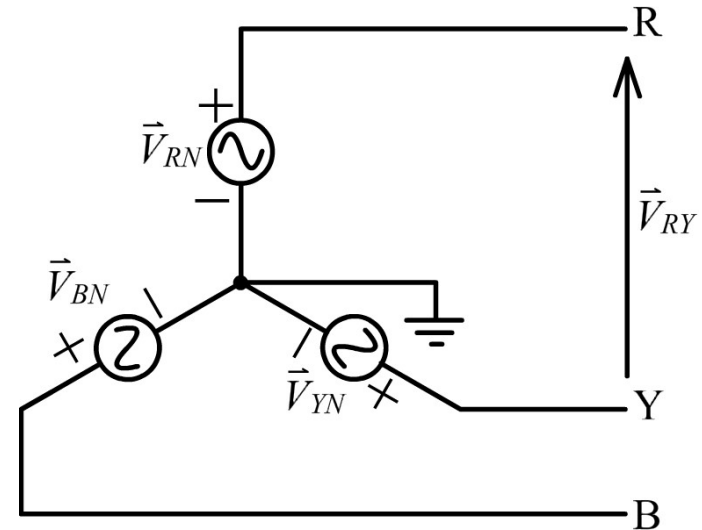

$$V_P = \frac{V_L}{\sqrt{3}}$$

$$V_P = \frac{380}{\sqrt{3}} = \underline{\underline{219.4 \text{ V}}}$$

Three-phase Circuit #1

- For the 3-phase circuit shown in Figure below, find the current in the neutral wire and the real power. (all values in rms)

Solution:

$$\vec{I}_A = \frac{\vec{V}_A}{50} = \frac{110\angle 0^\circ}{50} = 2.2\angle 0^\circ \text{ (A)}$$


$$\vec{I}_B = \frac{\vec{V}_B}{j45} = \frac{110\angle -120^\circ}{45\angle 90^\circ} = 2.44\angle -210^\circ \text{ (A)}$$

or $2.44\angle 150^\circ \text{ (A)}$

$$\vec{I}_C = \frac{\vec{V}_C}{-j20} = \frac{110\angle 120^\circ}{20\angle -90^\circ} = 5.5\angle 210^\circ \text{ (A)}$$

$$\begin{aligned}\vec{I}_N &= \vec{I}_A + \vec{I}_B + \vec{I}_C \\ &= 2.2\angle 0^\circ + 2.44\angle 150^\circ + 5.5\angle 210^\circ = 4.92\angle -161.9^\circ \text{ (A)}\end{aligned}$$

$$\text{Real Power} = |\vec{V}_A| |\vec{I}_A| = 110 \times 2.2 = 242 \text{ (W)}$$

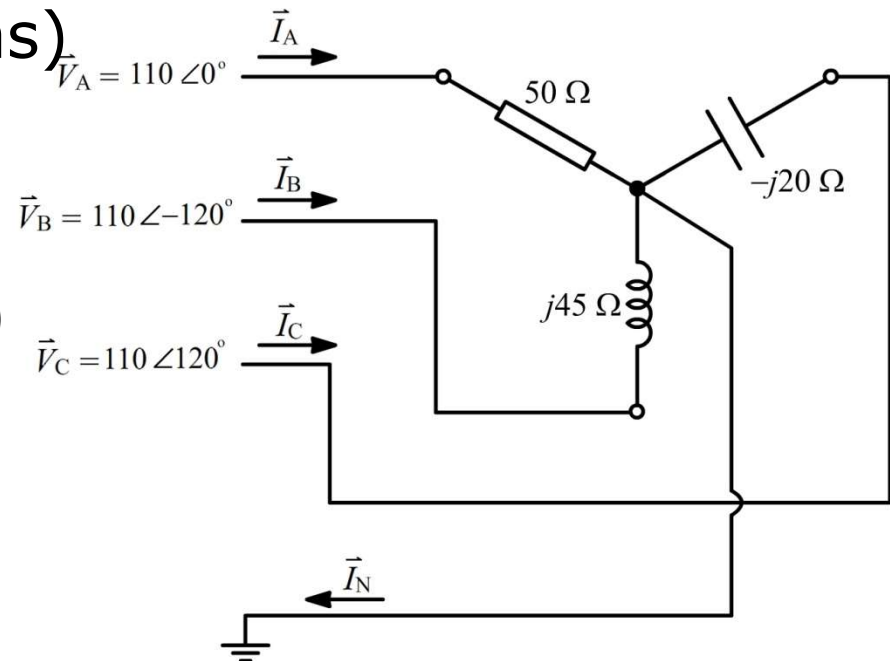

Three-phase Circuit #2

- Find the current in the neutral wire and the real power. (all values are in rms)


Solution:

$$\vec{I}_A = \frac{\vec{V}_A}{40 + j10} = \frac{220 \angle 0^\circ}{41.23 \angle 14.04^\circ} = 5.3358 \angle -14.04^\circ \text{ (A)}$$

$$\begin{aligned} \vec{I}_B &= \frac{\vec{V}_B}{20 - j5} = \frac{110 \angle -120^\circ}{20.6155 \angle -14.04^\circ} \\ &= 5.338 \angle -105.96^\circ \text{ (A)} \end{aligned}$$

$$\vec{I}_C = \frac{\vec{V}_C}{20 + j5} = \frac{110 \angle 120^\circ}{20.6155 \angle 14.04^\circ} = 5.3358 \angle 105.96^\circ \text{ (A)}$$
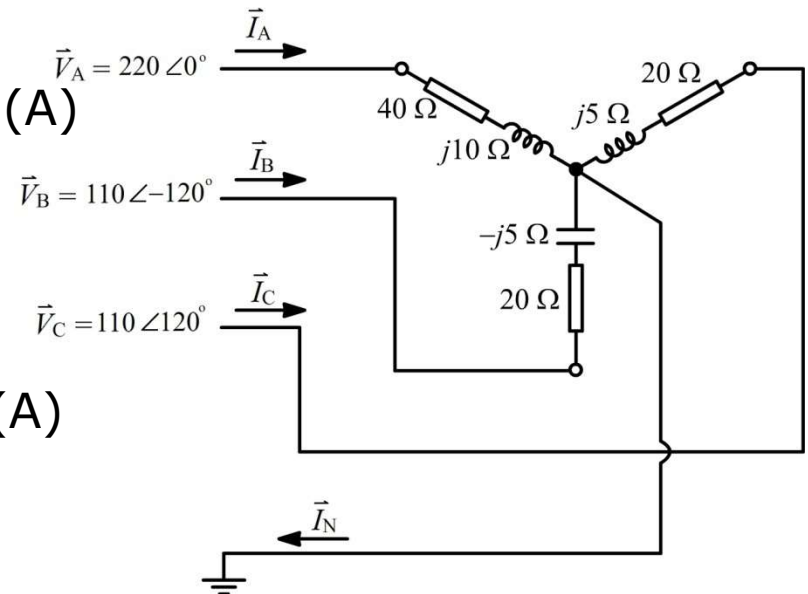
$$\begin{aligned} \vec{I}_N &= \vec{I}_A + \vec{I}_B + \vec{I}_C \\ &= 5.3358 \angle -14.04^\circ + 5.3358 \angle -105.96^\circ + 5.3358 \angle 105.96^\circ \\ &= 2.59 \angle -30^\circ \text{ (A)} \end{aligned}$$



$$P_C = |\vec{I}_C|^2 R_C = (5.3358)^2 (20) = 569.41 \text{ W}$$

Three-phase Circuit #2

Find the real power.

$$\vec{I}_A = 5.3358 \angle -14.04^\circ \text{ (A)}$$

$$\vec{I}_B = 5.3358 \angle -105.96^\circ \text{ (A)}$$


$$\vec{I}_C = 5.3358 \angle 105.96^\circ \text{ (A)}$$

$$P_A = |\vec{I}_A|^2 R_A = (5.3358)^2 (40) = 1138.8 \text{ (W)}$$

$$P_B = |\vec{I}_B|^2 R_B = (5.3358)^2 (20) = 569.41 \text{ (W)}$$

$$P_C = |\vec{I}_C|^2 R_C = (5.3358)^2 (20) = 569.41 \text{ (W)}$$
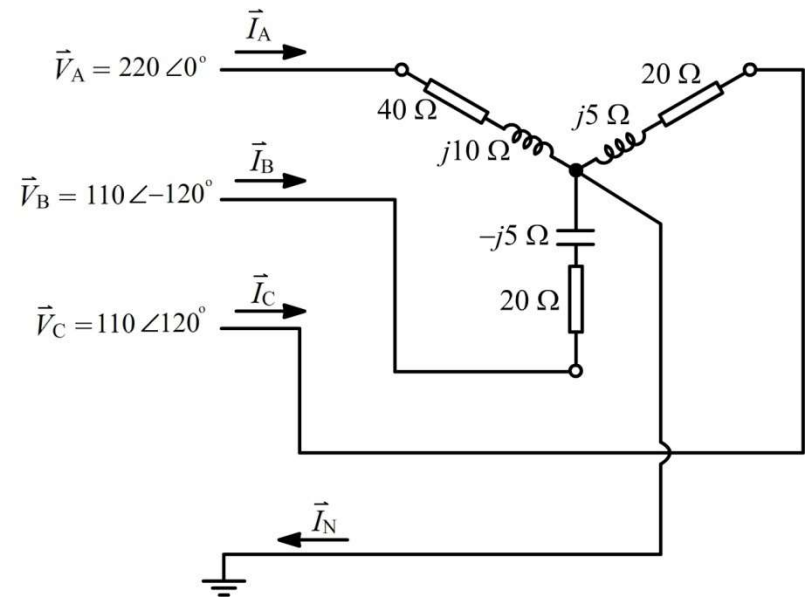
$$\begin{aligned} \text{Total real power} &= P_A + P_B + P_C \\ &= 1138.8 + 569.41 + 569.41 \\ &= \underline{\underline{2277.62 \text{ W}}} \end{aligned}$$



Three-phase Power

Find the current in the neutral wire.

(all values are in rms)

$$|S_A| \cos \theta_A = P_A = 5 \times 100$$

$$|S_A| = \frac{500}{p.f.} = \frac{500}{0.6} = 833.33$$

$$S_A = 833.33 \angle (\cos^{-1} 0.6) = \vec{V}_A \vec{I}_A^*$$

$$\vec{I}_A^* = \frac{833.33 \angle 53.13^\circ}{220 \angle 0^\circ} = 3.7879 \angle 53.13^\circ$$


$$\vec{I}_A = 3.7879 \angle -53.13^\circ$$

$$|S_B| = \frac{2 \times 20}{p.f.} = \frac{40}{0.8} = 50$$

$$S_B = 50 \angle (\cos^{-1} 0.8) = \vec{V}_B \vec{I}_B^*$$

$$\vec{I}_B^* = \frac{50 \angle 36.87^\circ}{220 \angle -120^\circ} = 0.2273 \angle 156.87^\circ$$
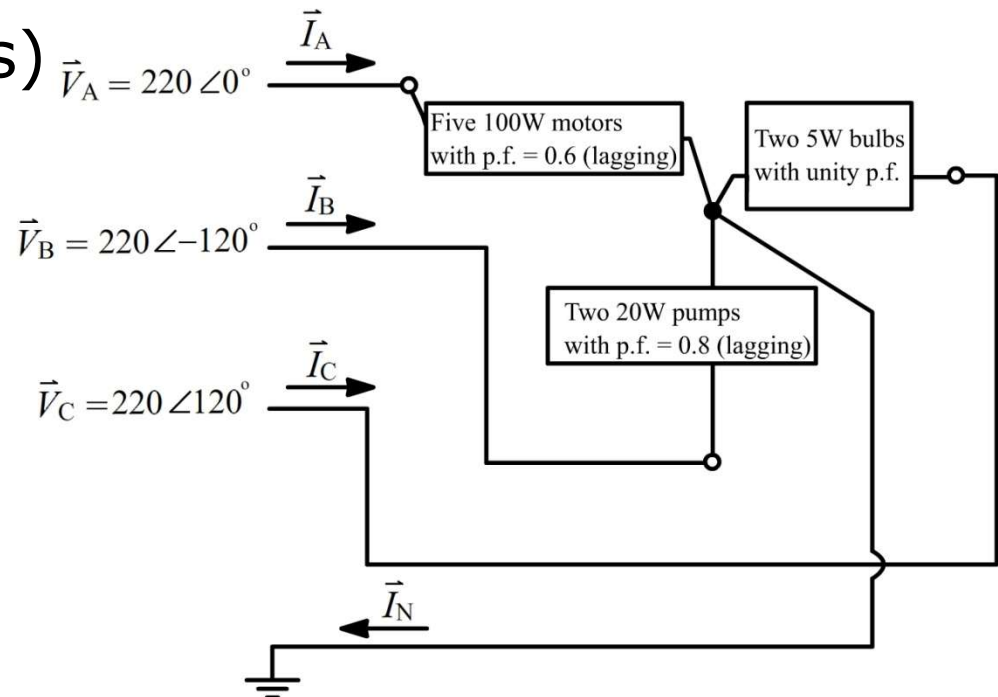
$$\vec{I}_B = 0.2273 \angle -156.87^\circ$$



$$|S_C| = \frac{2 \times 5}{p.f.} = \frac{10}{1} = 10 \Rightarrow S_C = 10 \angle 0^\circ = \vec{V}_C \vec{I}_C^*$$

$$\vec{I}_C^* = \frac{10 \angle 0^\circ}{220 \angle 120^\circ} = 0.04545 \angle -120^\circ$$


$$\vec{I}_C = 0.04545 \angle 120^\circ$$

Three-phase Power

$$\vec{I}_A = 3.7879 \angle -53.13^\circ$$

$$\vec{I}_B = 0.2273 \angle -156.87^\circ$$

$$\vec{I}_C = 0.04545 \angle 120^\circ$$

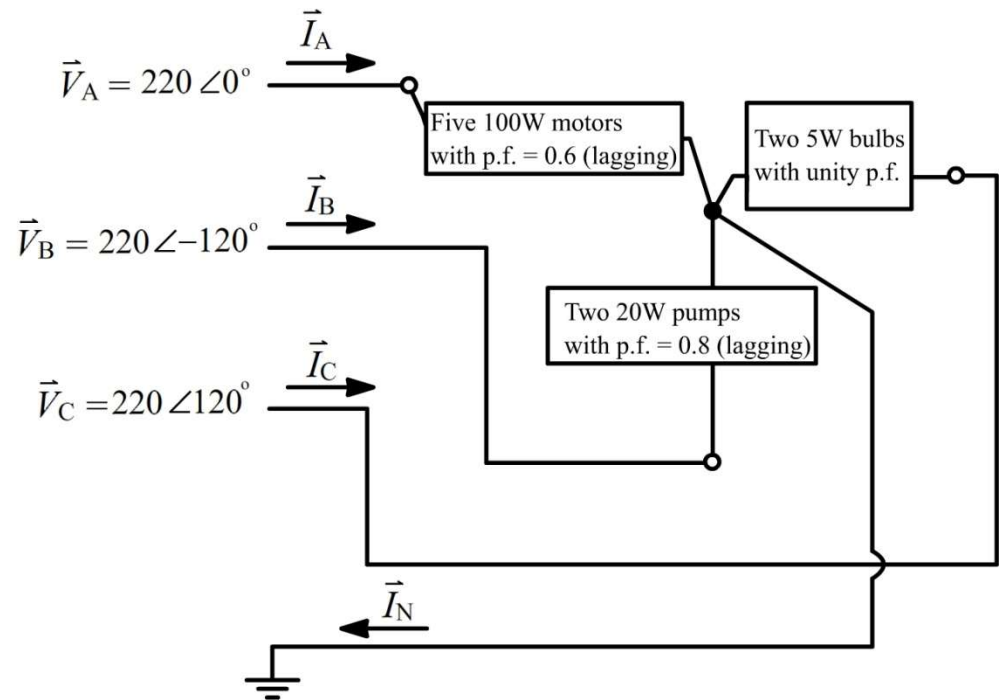

$$\vec{I}_N = \vec{I}_A + \vec{I}_B + \vec{I}_C$$

$$= 3.7879 \angle -53.13^\circ + 0.2273 \angle -156.78^\circ + 0.04545 \angle 120^\circ$$

$$= 3.695 \angle -56.47^\circ \text{ (A)}$$

Q22

The load Z_L consists of a $25\ \Omega$ resistor in series with a $0.1\ \text{mF}$ capacitor and a $70.35\ \text{mH}$ inductor. Assuming $f = 60\ \text{Hz}$, calculate the following

- The apparent power delivered to the load.
- The real (or active) power supplied by the source.
- The power factor of the load.

$$\omega = 2\pi f = 120\pi\ (\text{rad/sec})$$

$$Z_L = 25 + j\omega L + \frac{1}{j\omega C} = 25 - j0.0045 = 25\angle -0.01^\circ$$

$$\tilde{\mathbf{I}}_S = \frac{\tilde{\mathbf{V}}_S}{R + Z_L} = \frac{230\angle 0^\circ}{1 + 25 - j0.0045} = 8.846\angle 0.01^\circ$$


$$\tilde{\mathbf{V}}_L = \tilde{\mathbf{I}}_S Z_L = (8.846\angle 0.01^\circ)(25 - j0.0045) \approx 221.15\angle 0^\circ\ \text{V}$$

$$\mathbf{S}_L = \tilde{\mathbf{V}}_L \tilde{\mathbf{I}}_S^* = (221.15\angle 0^\circ)(8.846\angle -0.01^\circ) = 1956.36\angle -0.01^\circ\ \text{VA}$$

$$|\mathbf{S}_L| = 1956.36\ \text{VA}$$

$$\begin{aligned}\mathbf{S}_S &= \tilde{\mathbf{V}}_S \tilde{\mathbf{I}}_S^* = (230\angle 0^\circ)(8.846\angle -0.01^\circ) = 2034.6\angle -0.01^\circ \\ &= \boxed{2034.615} - j0.352\ \text{VA}\end{aligned}$$
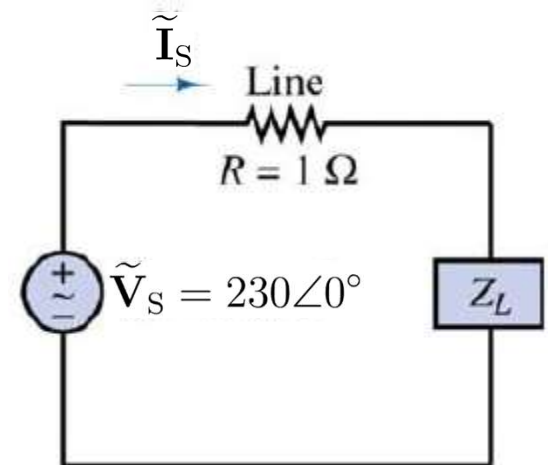
$$\text{Real power} = 2034.615\ \text{W}$$




$$\begin{aligned}\text{Power factor of the load} \\ &= \cos(-0.01^\circ) \approx 1.0\end{aligned}$$

Q23

A $230 \text{ V}_{\text{rms}}$ source has two loads connected to it in parallel. One draws 8 kVA at lagging power factor of 0.9 , and the other draws 10 kW at a lagging power factor of 0.8 .

- Find the rms source current amplitude.
- At what power factor is the source operating?

Since we only need to find amplitude of $\tilde{\mathbf{I}}_S$,
we may assume source voltage having angle of 0° .

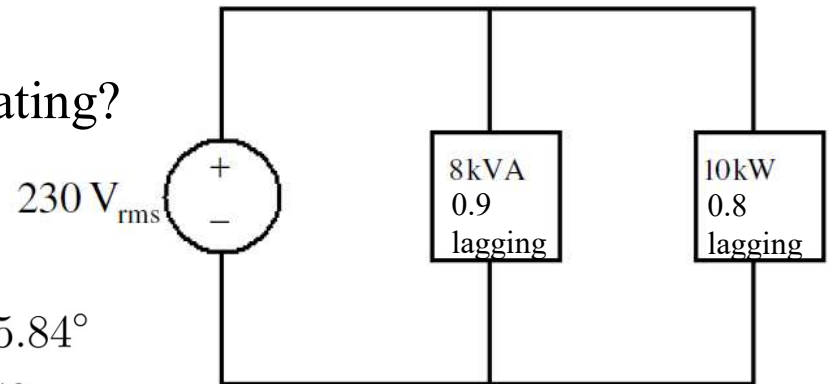

Load 1: p.f. of load1 = $\cos(\theta_1) = 0.9 \Rightarrow \theta_1 = 25.84^\circ$

$$\mathbf{S}_1 = \tilde{\mathbf{V}}_S \tilde{\mathbf{I}}_1^* \Rightarrow \tilde{\mathbf{I}}_1^* = \frac{\mathbf{S}_1}{\tilde{\mathbf{V}}_S} = \frac{8000 \angle 25.84^\circ}{230 \angle 0^\circ} = 34.7826 \angle 25.84^\circ$$

Load 2: p.f. of load2 = $\cos(\theta_2) = 0.8 \Rightarrow \theta_2 = 36.87^\circ$

$$\mathbf{S}_2 = \tilde{\mathbf{V}}_S \tilde{\mathbf{I}}_2^* \Rightarrow \tilde{\mathbf{I}}_2^* = \frac{\mathbf{S}_2}{\tilde{\mathbf{V}}_S} = \frac{\left(\frac{10000}{0.8}\right) \angle 36.87^\circ}{230 \angle 0^\circ} = 54.3478 \angle 36.87^\circ$$


$$\tilde{\mathbf{I}}_S = \tilde{\mathbf{I}}_1 + \tilde{\mathbf{I}}_2 = (34.7826 \angle -25.84^\circ) + (54.3478 \angle -36.87^\circ) = 88.7377 \angle -32.57^\circ$$

The rms source current amplitude = $88.7377 \text{ A}_{\text{rms}}$

$$\mathbf{S}_S = \tilde{\mathbf{V}}_S \tilde{\mathbf{I}}_S^* \Rightarrow \text{p.f. of the source} = \cos(32.57^\circ) = 0.8427 \text{ lagging}$$

AC Maximum Real Power Transfer

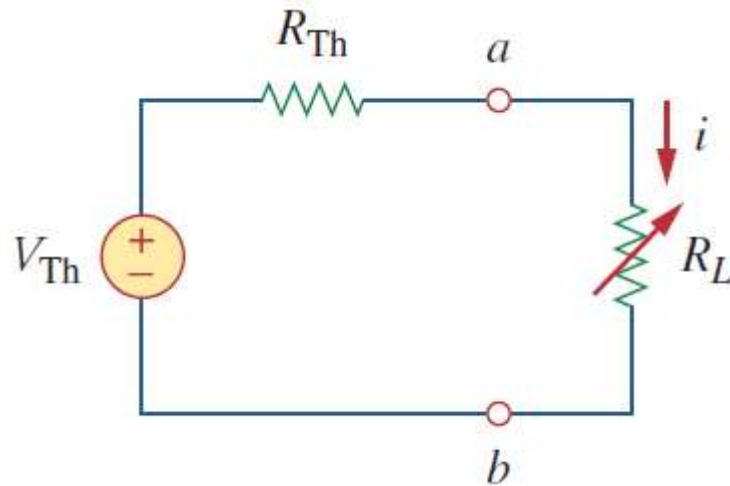
- For DC, max. power transfer occurs when $R_L = R_{Th}$:



$$p = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

$$p_{max} = \frac{V_{Th}^2}{4R_{Th}}$$

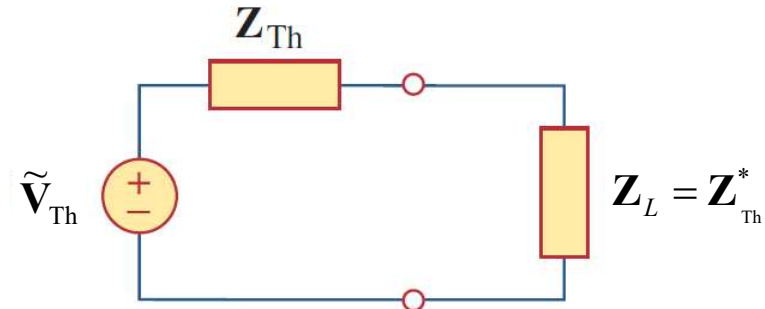- For AC, max. power transfer occurs when $Z_L = Z_{Th}^*$,
 Z_{Th}^* is complex conjugate of Z_{Th}



If $Z_{Th} = 5 + j4$ and $Z_L = 5 - j4$, max. power transfer occurs.

Complex power from source is real.

$$S_{source} = \tilde{V}_{Th} \tilde{I}^* = \left(\tilde{V}_{Th} \left(\frac{\tilde{V}_{Th}}{Z_{Th} + Z_L} \right)^* \right) = \left(\tilde{V}_{Th} \left(\frac{\tilde{V}_{Th}}{5 + 5} \right)^* \right) = \frac{\tilde{V}_{Th} \tilde{V}_{Th}^*}{10}$$

As an example, when $\tilde{V}_{Th} = 220 \angle 25^\circ$ (Vrms)

$$S_{source} = \frac{\tilde{V}_{Th} \tilde{V}_{Th}^*}{10} = \frac{(220 \angle 25^\circ)(220 \angle -25^\circ)}{10} = 4840 \angle 0^\circ$$

Voltage source supplies real power = 4840 W

AC Maximum Real Power Transfer

Voltage source supplies real power = 4840 W

Since only resistors absorb real power,
the two 5 Ω resistors share 4840 W:

Max. real power absorbed by $Z_L = \underline{2420 \text{ W}}$

Check this result by $S_L = \tilde{V}_L \tilde{I}_L^*$

$$S_L = \left(\frac{Z_L}{Z_{Th} + Z_L} \tilde{V}_{Th} \right) \left(\frac{\tilde{V}_{Th}}{Z_{Th} + Z_L} \right)^* = \frac{(5 - j4) \tilde{V}_{Th} \tilde{V}_{Th}^*}{100}$$

$$S_L = \frac{(5 - j4)(220 \angle 25^\circ)(220 \angle -25^\circ)}{100} = 2420 - j1936$$


Max. real power absorbed by $Z_L = 2420 \text{ W}$

OR use the DC formula :

$$P_{L, \max} = \frac{|\tilde{V}_{Th}|^2}{4R_{Th}} = \frac{220^2}{4 \times 5} = 2420 \text{ W}$$

$$p_{max} = \frac{V_{Th}^2}{4R_{Th}}$$

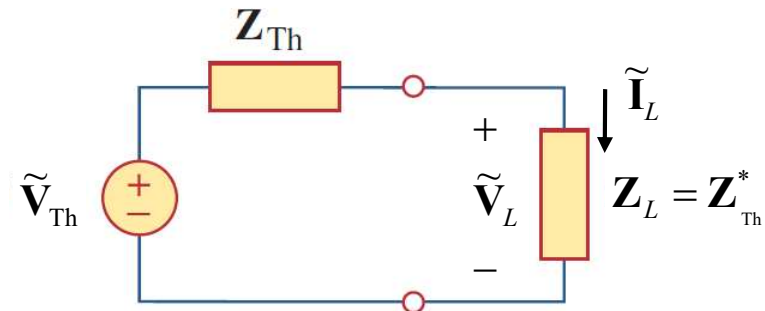- For AC, max. power transfer occurs when $Z_L = Z_{Th}^*$,
 Z_{Th}^* is complex conjugate of Z_{Th}



$$Z_{Th} = 5 + j4$$

$$Z_L = 5 - j4$$

$$S_{\text{source}} = \tilde{V}_{Th} \tilde{I}^* = \left(\tilde{V}_{Th} \left(\frac{\tilde{V}_{Th}}{Z_{Th} + Z_L} \right) \right)^* = \left(\tilde{V}_{Th} \left(\frac{\tilde{V}_{Th}}{5 + 5} \right) \right)^* = \frac{\tilde{V}_{Th} \tilde{V}_{Th}^*}{10}$$

As an example, when $\tilde{V}_{Th} = 220 \angle 25^\circ \text{ (Vrms)}$

$$S_{\text{source}} = \frac{\tilde{V}_{Th} \tilde{V}_{Th}^*}{10} = \frac{(220 \angle 25^\circ)(220 \angle -25^\circ)}{10} = 4840 \angle 0^\circ$$